
 


Memory

Computer Engineering 2

Motivation

Storing and retrieving data

 

- **Memory Technologies**
 - PROM, EEPROM and flash, SRAM, SDRAM
- **On-CHIP Memories STM32F429ZISRAM**
 - SRAM and Flash
- **External Memory (Off-Chip)**
 - Flexible Memory Controller
- **Appendix: Trends and Figures**


Learning Objectives

At the end of this lesson, you will be able

- to classify widely used memory technologies
- to discuss the structure and function of an SRAM (static RAM)
- to discuss the structure and function of flash memory
- to outline the structure and function of an asynchronous SRAM device
- to outline how an external asynchronous SRAM device can be connected through the flexible memory controller (FMC)
- to explain how an internal 32-bit access is partitioned into several external half-word or byte accesses
- to interpret timing diagrams for read and write accesses to external, asynchronous SRAMs
- to summarize the differences between a NOR and a NAND flash
- to summarize the differences between a static RAM (SRAM) and a dynamic RAM (SDRAM)

Semiconductor Fundamentals

MEMORY TECHNOLOGIES

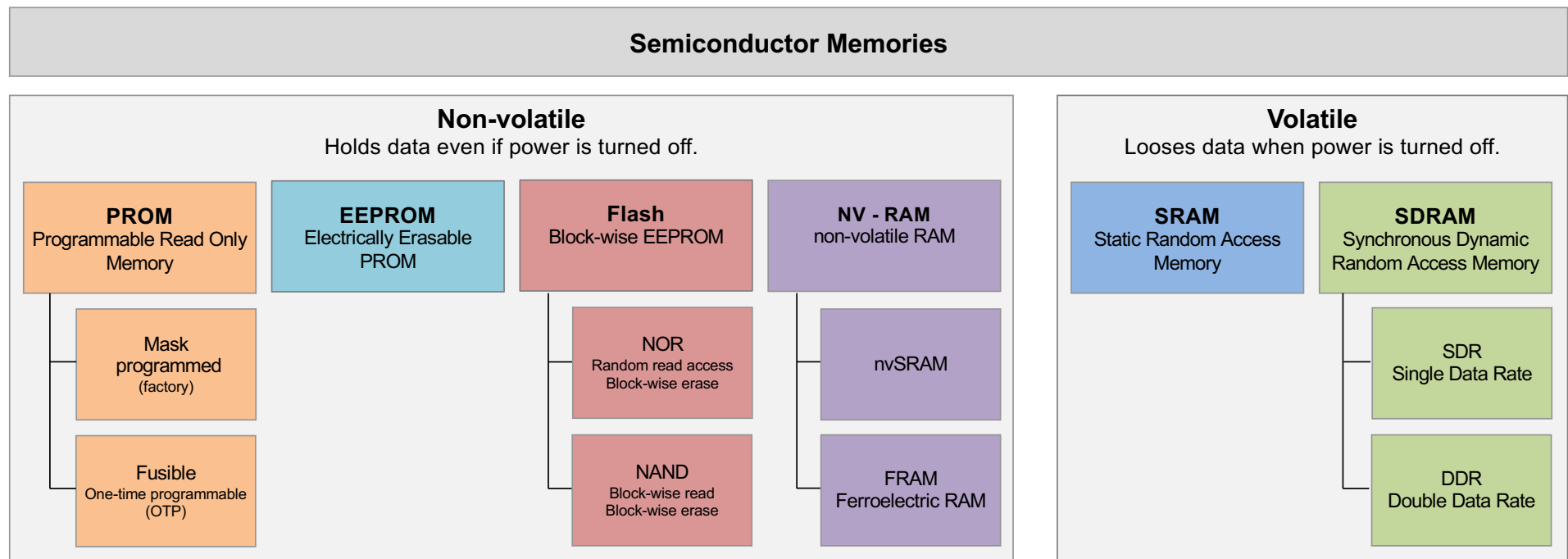

■ Unit Symbols

- b = bit B = Byte

■ Memory Chips

- Binary prefixes according to JEDEC¹⁾ and IEC²⁾
 - Kilo K = 1024
 - Mega M = 1024 x 1024 = 1'048'510
 - Giga G = 1024 x 1024 x 1024 = 1'073'741'824
 - Tera T = 1024 ^ 4 = 1'099'511'627'776 (nearly 10 % more than SI prefix)

■ Hard Disks

- Often use SI (or metric) prefixes
 - Kilo k = 1000
 - Mega M = 1000 x 1000
 - Giga G = 1000 x 1000 x 1000
 - Tera T = 1000 ^ 4


1) JEDEC Solid State Technology Association
2) International Electrotechnical Commission

Memories Are Arrays of Bit Cells

■ Memory Architecture → $n \times m$ array

■ Bit cell → stores '1' or '0'

- n words with m data bits

 


PROM – Programmable Read Only Memory

■ $n \times m$ array

n = number of word lines
 m = number of bit lines

→ n addresses with m data bits

Example 512 x 4 bit

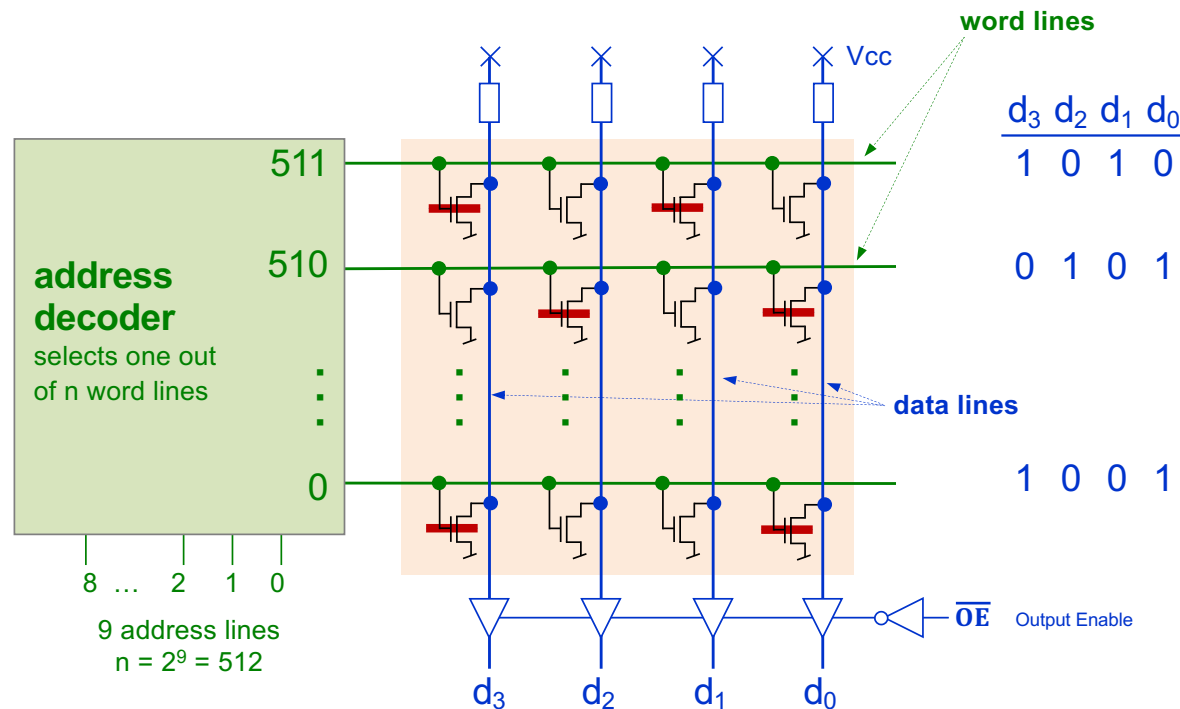

Fusible Transistors
Programming applies higher voltage to destroy transistors (blow fuses)
Process is not reversible



Word line = '1'
→ transistor shortens bit line to GND
Word line = '0'
→ transistor open; pull-up pulls bit to V_{cc}

Transistor destroyed (fused)
→ always open, i.e. pull-up pulls bit line to V_{cc}


EEPROM and Flash

■ Making PROMs Reprogrammable

- "Floating Gate" transistor
 - Replace fusing by reprogrammable "Floating Gate"
- Write cell to '0' → **ON**
 - High voltage Up deposits charge on floating gate (isolated by SiO₂)
 - Transistor ON (conducting) if control gate equal '1'
- Erase cell to '1' → **OFF**
 - Discharge floating gate with negative Up
 - Transistor is OFF, i.e. blocking independent of value on control gate
- EEPROM
 - High cell area → low density, high cost per bit
- Flash
 - Erasing can only be done for whole sectors
→ small cell area, high density, low cost per bit

 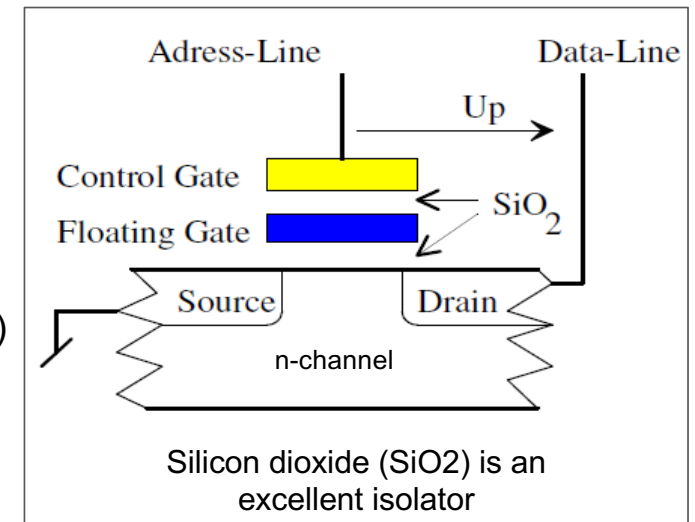


 ■ Use 'Floating Gates' instead of 'Fusible Transistors'



■ Write Operations (Programming)

 - Can only change bits from '1' to '0'
 - Otherwise, an erase operation is required
- Word, half-word or byte access possible
- Writing a double word ~16 us
 - I.e. around 1000 times slower than SRAM





■ Erase Operations

- Change all bits from '0' to '1'
 - **Only possible by sector or by bank**, not on a word
 - Typical sector sizes of 16
- Erase of a 128 Kbytes sector takes between 1 and 2 seconds ¹⁾
- Endurance: 10'000 erase cycles ²⁾
- Sector may not be accessed (write or read) during erase
 - I.e. execute program from another sector or from SRAM during erase


1) Depending on supply voltage and configuration parameters
2) Value from STM32F429ZI datasheet

Flash – NOR vs NAND Topology

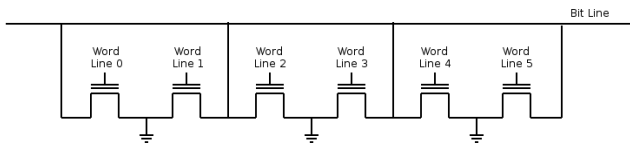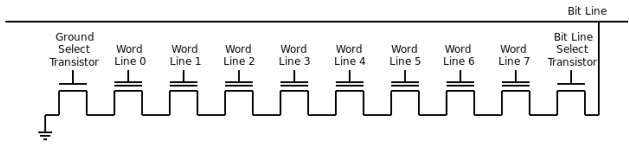	NOR Flash	NAND Flash
Topology	 <p>The diagram shows a NOR Flash topology. A horizontal Bit Line is connected to a series of vertical Word Lines (Word Line 0 to Word Line 5). Each Word Line has a transistor connected to the Bit Line. The transistors are connected in a way that allows for random access to individual bytes.</p>	 <p>The diagram shows a NAND Flash topology. A horizontal Bit Line is connected to a series of vertical Word Lines (Word Line 0 to Word Line 7). Each Word Line has a transistor connected to the Bit Line. The transistors are connected in a way that allows for sequential access to data in blocks.</p>
Applications	<ul style="list-style-type: none"> • Execute code directly from memory • Persistent device configurations (replacement of EEPROM) 	<ul style="list-style-type: none"> • File-based IO, disks • Large amounts of sequential data (images, SD cards, SSD) • Load programs into RAM before executing
Density	<ul style="list-style-type: none"> • Medium Up to 2 GBit = 256 MByte 	<ul style="list-style-type: none"> • High Up to 1 Tbit
Interface	<ul style="list-style-type: none"> • Read same as asynchronous SRAM • Types with serial interface available 	<ul style="list-style-type: none"> • Special NAND flash interface • Error correction for defective blocks
Access	<ul style="list-style-type: none"> • Random access read $\sim 0.12 \mu\text{s}$ • Writing individual bytes possible • Slow writes $\sim 180 \mu\text{s} / 32 \text{ Byte}$ 	<ul style="list-style-type: none"> • Slow random access read: 1. Byte $25 \mu\text{s}$, then $0.03 \mu\text{s}$ each • Writing of individual bytes difficult • Fast block write $\sim 300 \mu\text{s} / 2^{112} \text{ Bytes}$

SRAM – Static Random Access Memory

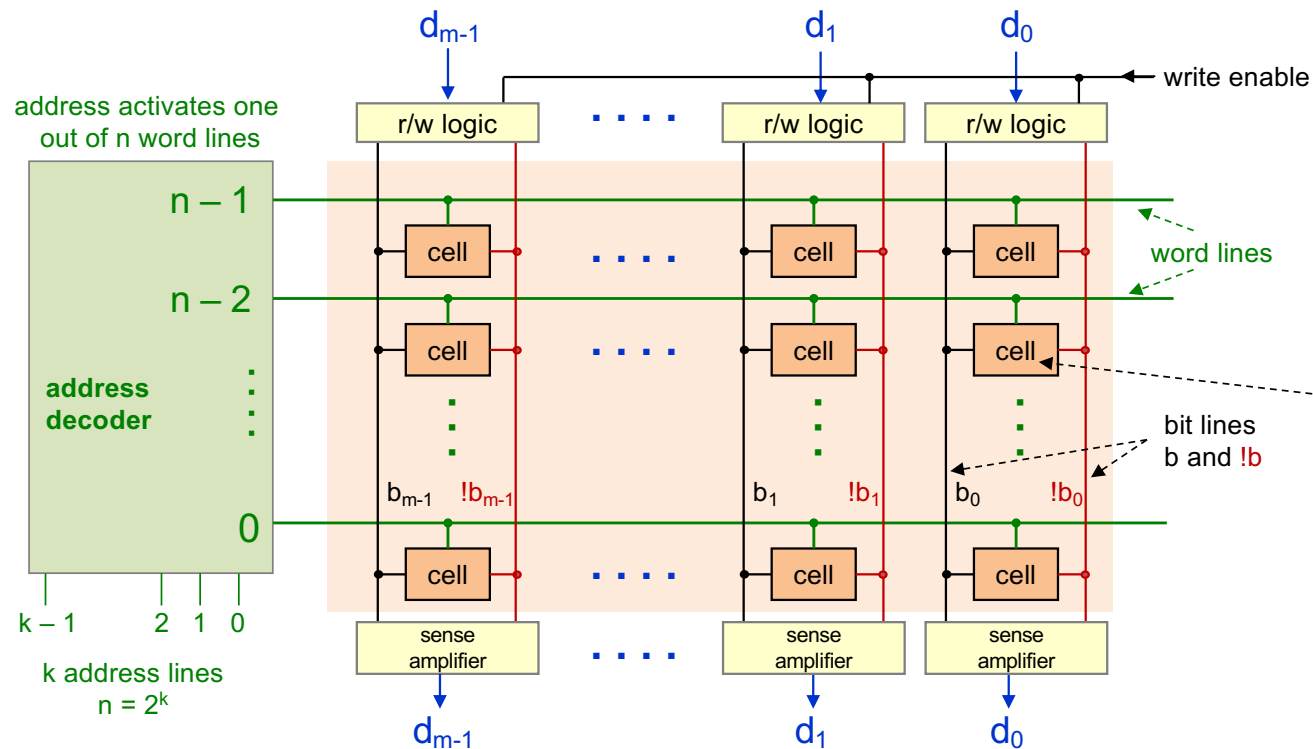■ $n \times m$ SRAM Architecture → flip-flop (latch) based cells



Example for NMOS: N-type metal-oxide-semiconductor logic

SRAM – Static Random Access Memory


Writing a Row (Word)

Set bit lines b and $!b$ to (1, 0) or (0, 1) respectively

Set the addressed word line to 1

Data is stored in cells

Set word line to 0

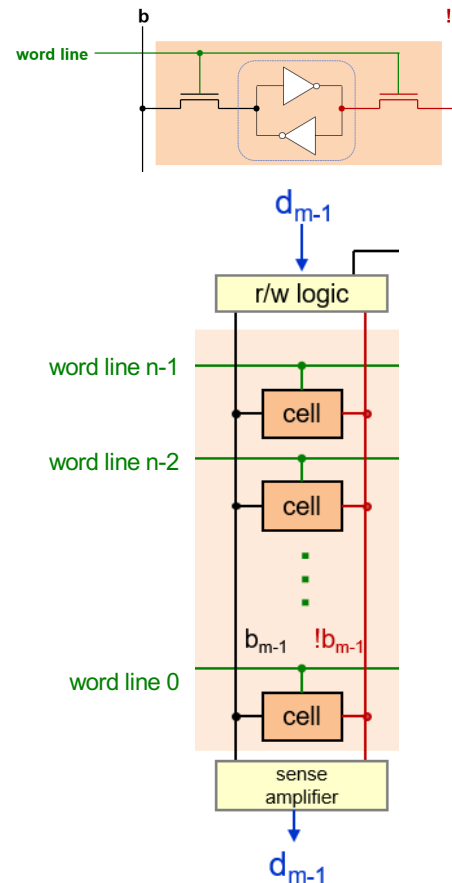

Reading a Row (Word)

Pre-charge both bit lines b and $!b$ to 1

Briefly set word line to 1


Inverters pull either b or $!b$ towards (not to) ground

Sense amplifier amplifies small voltage difference between lines b and $!b$

SRAM – Static Random Access Memory

■ Structure of SRAM cell in NMOS¹⁾

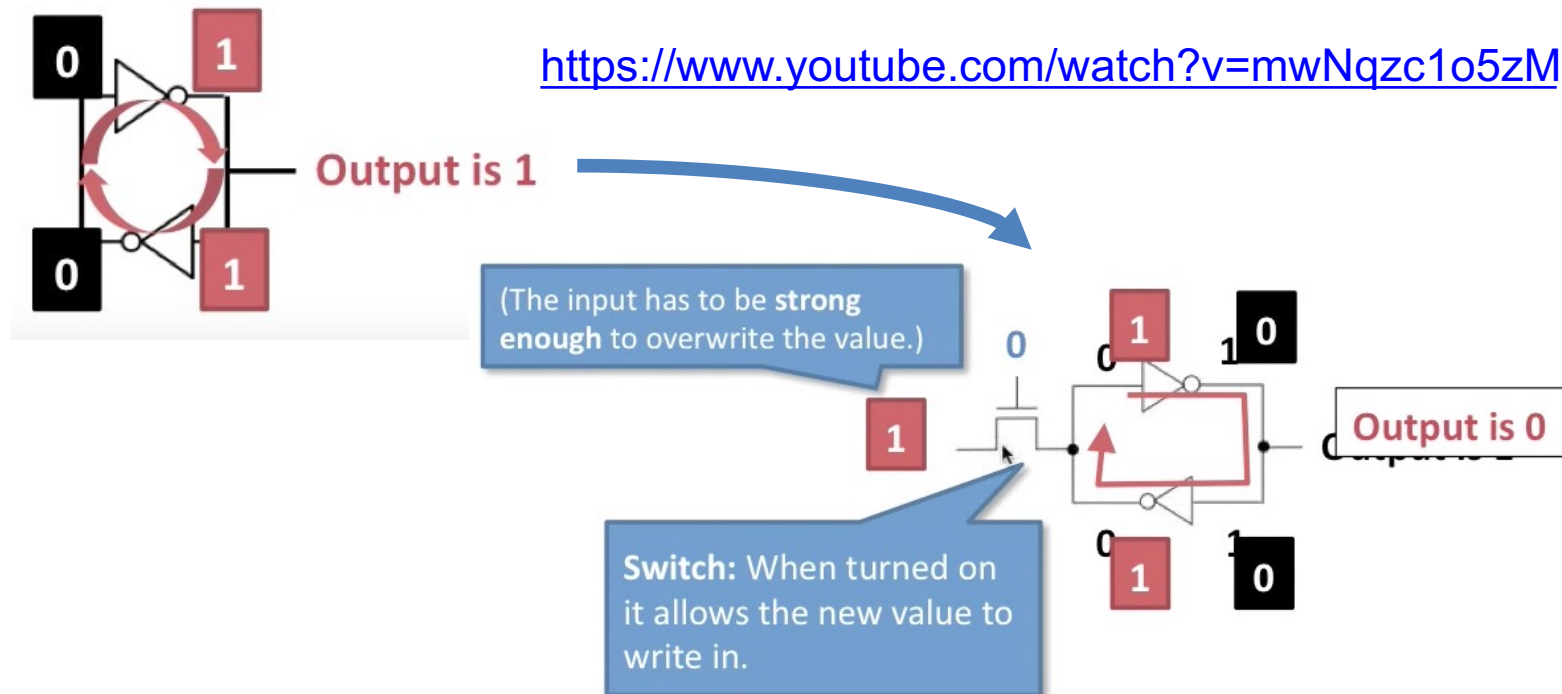- Flip-flop (latch) based structure, change from '1' to '0'



SRAM – Static Random Access Memory

■ Read and write

- All accesses take roughly the same time
- Access time independent of location of data item in memory
- Access time independent of previous access¹⁾

■ Volatile

- Memory content retained only as long as device is powered


■ Static

- Storage elements similar to flip-flops / latches
- No refresh required
 - refresh: periodic reading and rewriting of memory cell to maintain the content

1) as opposed to a DRAM that favors burst accesses

■ Asynchronous SRAM Device


- No clock input

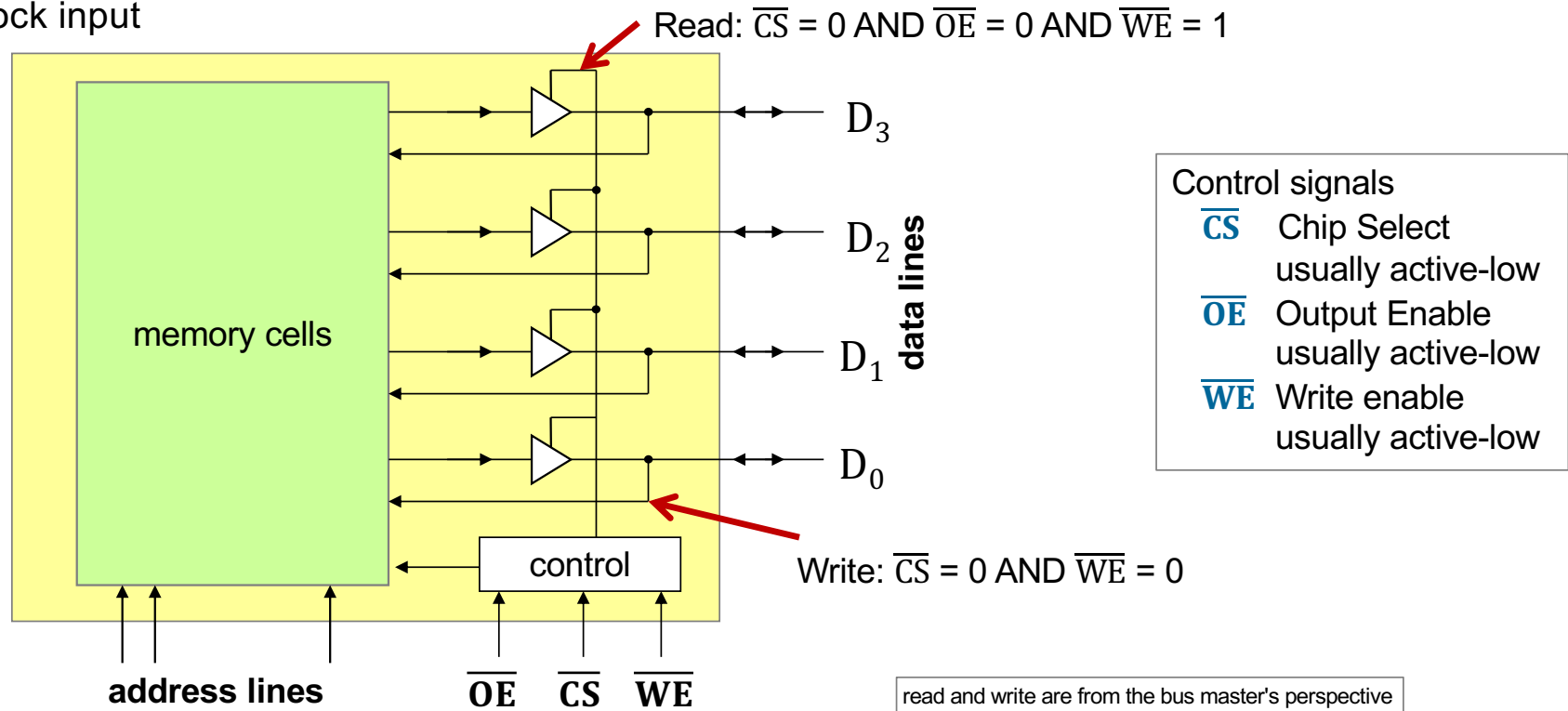

Asynchronous SRAM

■ Asynchronous SRAM Device

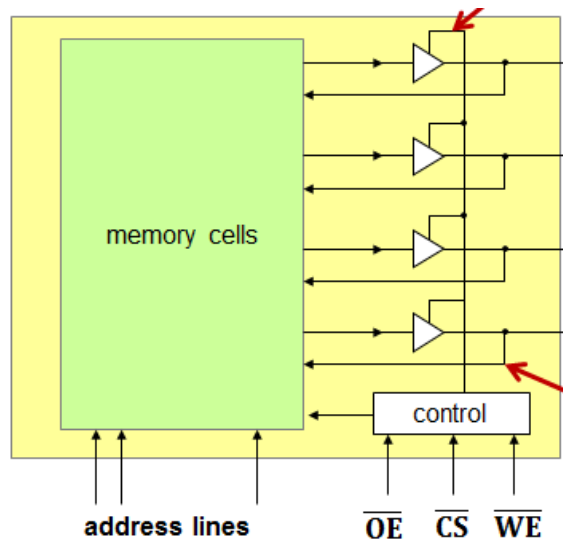- I.e. the device does not have a clock signal.



Alternatively the control logic can be represented with a truth table


\overline{CS}	\overline{OE}	\overline{WE}	I/O	Function
L	L	H	DATA OUT	Read Data
L	X	L	DATA IN	Write Data
L	H	H	HIGH-Z	Outputs Disabled
H	X	X	HIGH-Z	Deselected

Some memory vendors call the signal \overline{CE} (chip enable) instead of \overline{CS}

Asynchrones SRAM


Read Access

Timing Waveform of Read Cycle No. 1⁽¹⁾

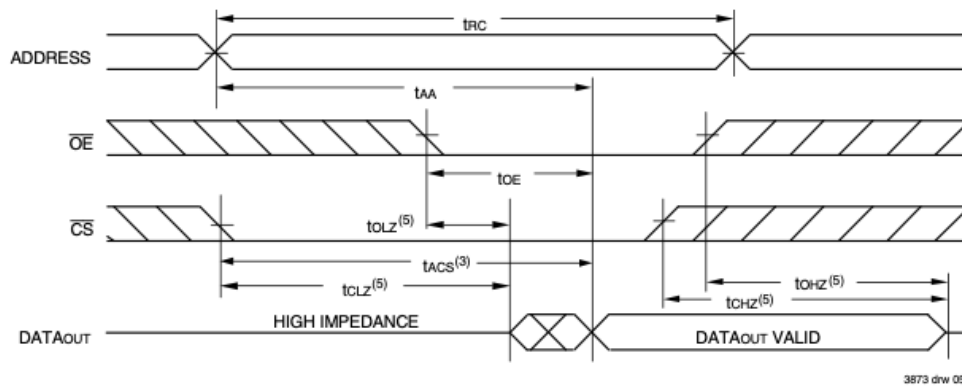

Write Access

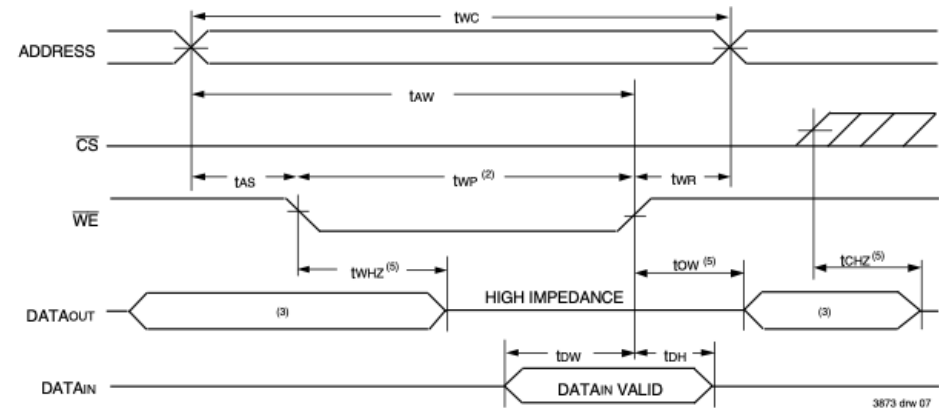Timing Waveform of Write Cycle No. 1 (\overline{WE} Controlled Timing)^(1,2,4)






SDRAM – Synchronous Dynamic RAM

External Chip

■ Synchronous Dynamic Random Access Memory

   - Information stored as charge in capacitor
- High integration
 - Large memories at low cost
 - Allows to store large amounts of data
- Leakage current → Loss of charge
 - Capacitor holds charge only for a few milliseconds
 - Charge has to be refreshed periodically → dynamic
 - Refresh logic usually located on SDRAM device



Trench Cell


<https://www.youtube.com/watch?v=3s7zsLU83bY>

SDRAM – Synchronous Dynamic RAM

External Chip

■ SDRAM Structure

- Row and column addresses multiplexed


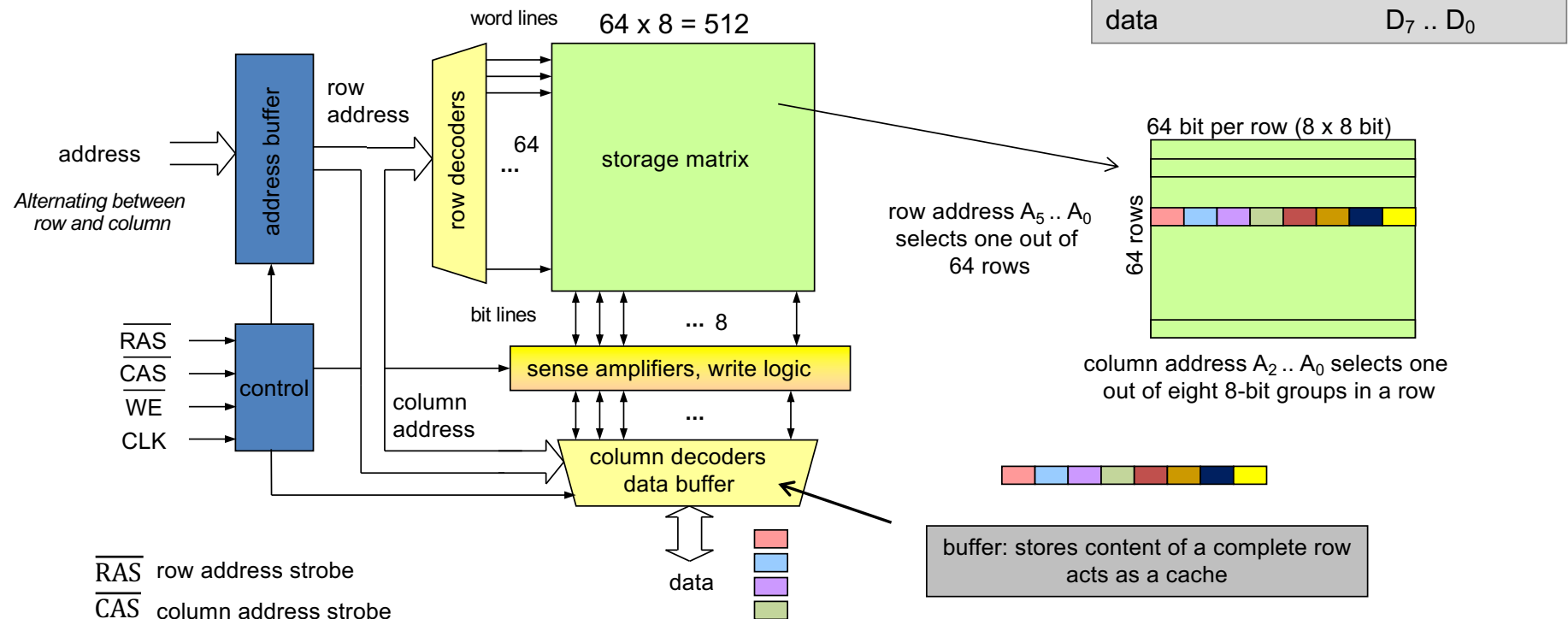


SDRAM – Synchronous Dynamic RAM

External Chip

■ Synchronous Interface

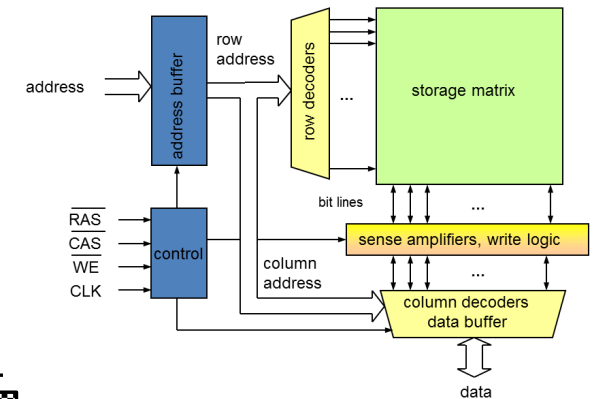
 
- Multiplexed row and column addresses
- Clocks up to 1200 MHz




$\overline{\text{RAS}}$ low → The master places the 6-bit row address on lines A[5:0].
 $\overline{\text{CAS}}$ low → The master places the 3-bit column address on lines A[2:0]. Lines A[5:3] are unused.

SDRAM – Synchronous Dynamic RAM

External Chip

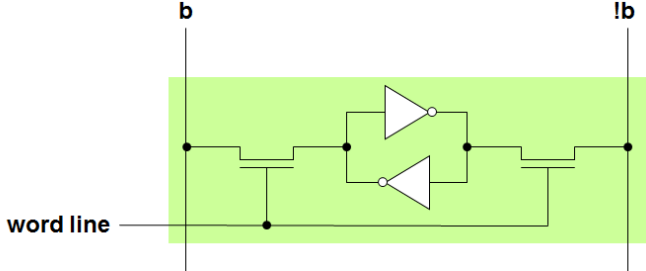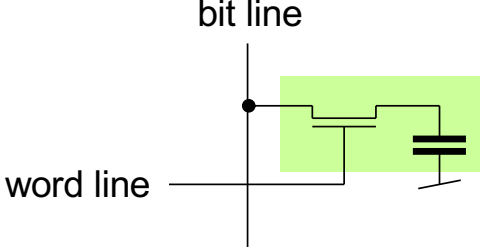Static RAM (SRAM)	Synchronous Dynamic RAM (SDRAM)
Flip-flop/latch → 4 Transistors / 2 resistors 	Transistor and capacitor 
Large cell <ul style="list-style-type: none">• Low density, high cost• Up to 64 Mb per device	Small cell <ul style="list-style-type: none">• High density, low cost• Up to 4 Gb per device
Almost no static power consumption <ul style="list-style-type: none">• Static i.e. no accesses taking place	Leakage currents <ul style="list-style-type: none">• Requires periodic refresh
Asynchronous interface (no clock) <ul style="list-style-type: none">• Simple connection to bus	Synchronous interface (clocked) <ul style="list-style-type: none">• Requires dedicated SDRAM Controller
All accesses take roughly the same time <ul style="list-style-type: none">• ~5ns per access → 200 MHz• Suitable for distributed accesses	Long latency for first access of a block <ul style="list-style-type: none">• Fast access for blocks of data (bursts)• Large overhead for single byte

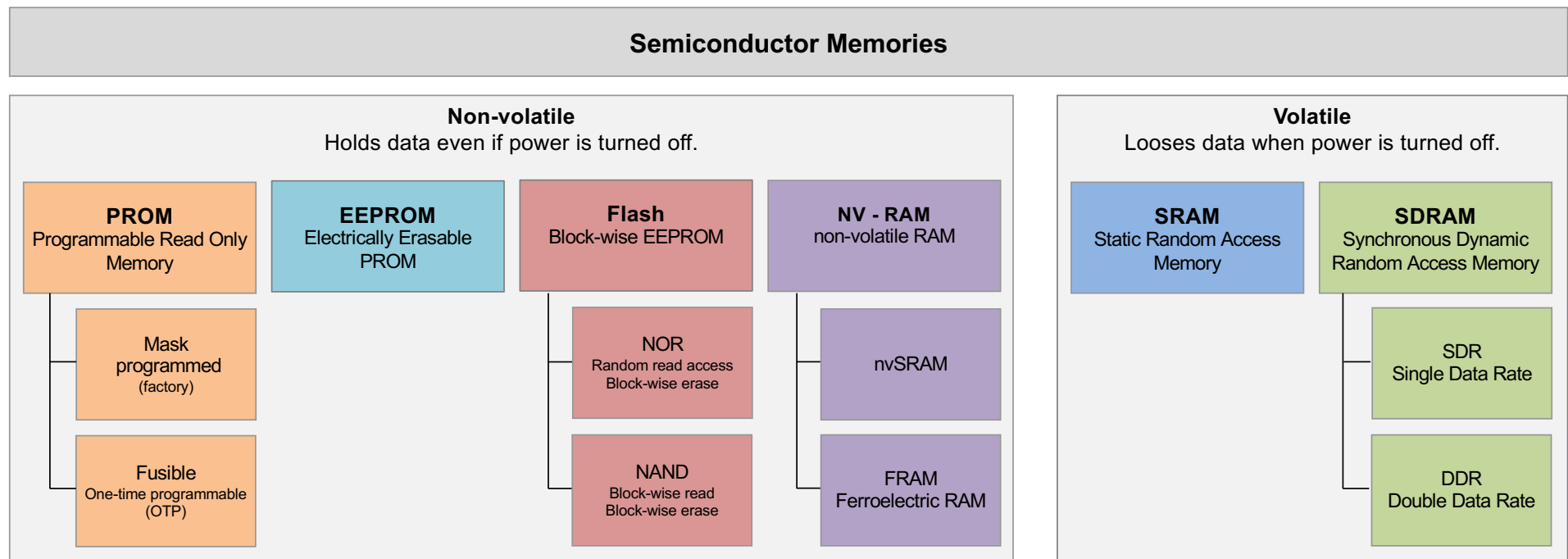


Our System

ON-CHIP MEMORIES STM32F429ZI

■ Simplified Model STM32F429ZI

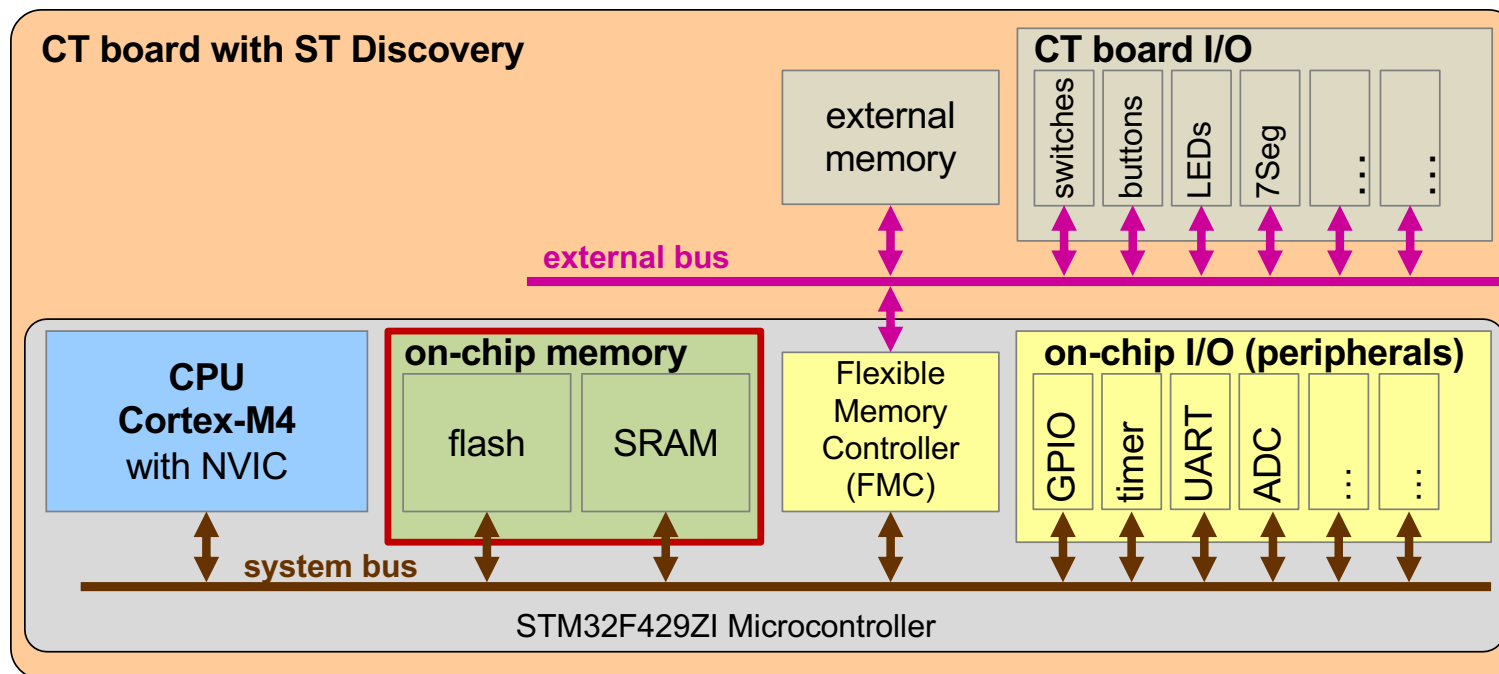- On-chip system bus 32 data lines, 32 address lines and control signals




On-chip Memory: SRAM

■ Address Regions

- SRAM1 112K bytes
- SRAM2 16K bytes
- SRAM3 64K bytes
- CCM 64K bytes

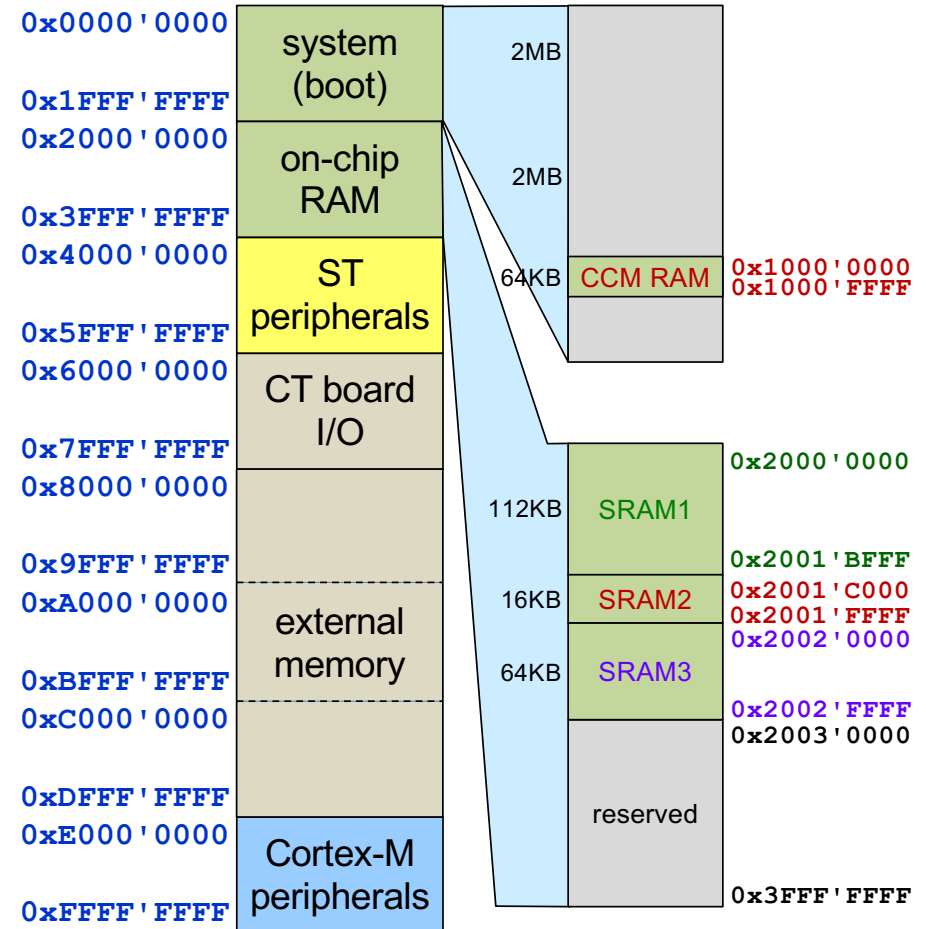CCM: Core Coupled Memory –
Fast memory exclusively addressable by the CPU.




On-chip Memory: Flash

■ Flash

- Non-volatile memory
 - Memory content retained after power off
- Store code and persistent data
- NOR topology
 - Like most on-chip flash memories

Persistent Data denotes information that is infrequently accessed and not likely to be modified.

Source: Wikipedia

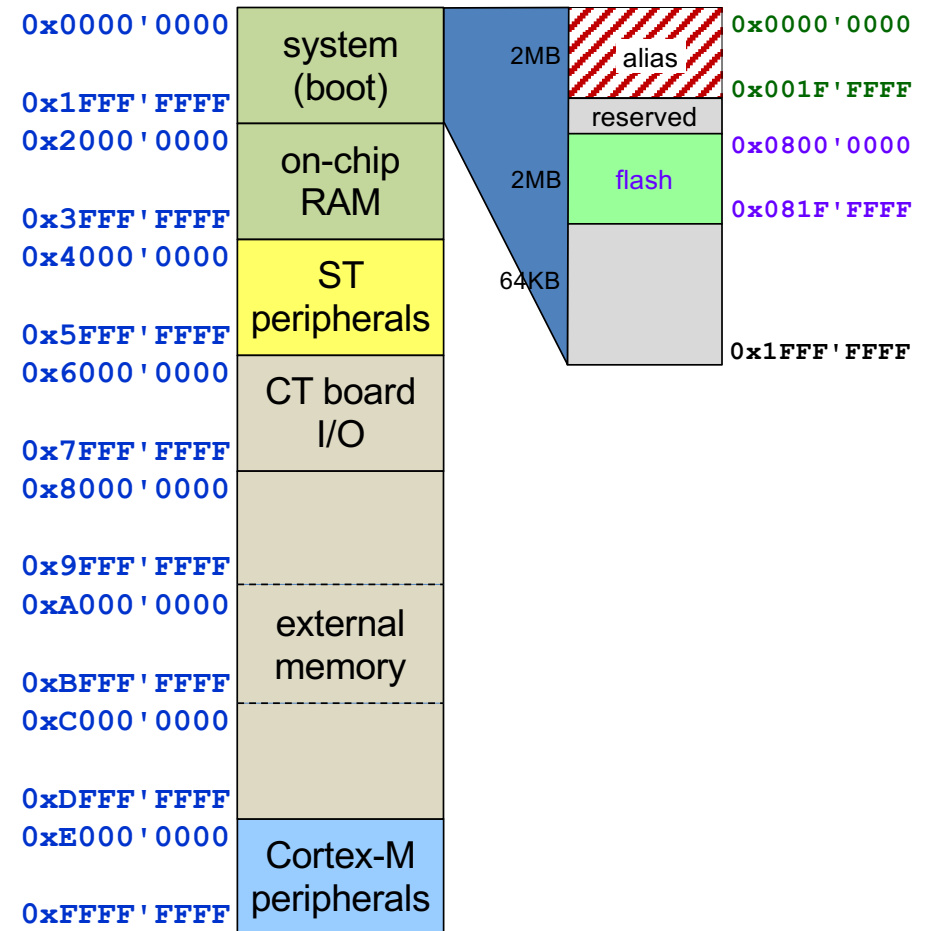

■ Flash Is Partitioned into Sectors


- Sectors can only be erased as a whole
- Writing through control registers – no direct memory write accesses

STM32F429ZI	Bank 1	Sector 0	0x0800'0000 – 0x0800'3FFF	16 Kbytes	total 2 Mbytes
		Sector 1	0x0800'4000 – 0x0800'7FFF	16 Kbytes	
		Sector 2	0x0800'8000 – 0x0800'BFFF	16 Kbytes	
		Sector 3	0x0800'C000 – 0x0800'FFFF	16 Kbytes	
		Sector 4	0x0801'0000 – 0x0801'FFFF	64 Kbytes	
		Sector 5	0x0802'0000 – 0x0803'FFFF	128 Kbytes	
		
		Sector 11	0x080E'0000 – 0x080F'FFFF	128 Kbytes	
	Bank 2	Sector 12	0x0810'0000 – 0x0810'3FFF	16 Kbytes	
		Sector 13	0x0810'4000 – 0x0810'7FFF	16 Kbytes	
		Sector 14	0x0810'8000 – 0x0810'BFFF	16 Kbytes	
		Sector 15	0x0810'C000 – 0x0810'FFFF	16 Kbytes	
		Sector 16	0x0811'0000 – 0x0811'FFFF	64 Kbytes	
		Sector 17	0x0812'0000 – 0x0813'FFFF	128 Kbytes	
		
		Sector 23	0x081E'0000 – 0x081F'FFFF	128 Kbytes	

On-chip Memory: Flash

■ Flash Has Higher Latency

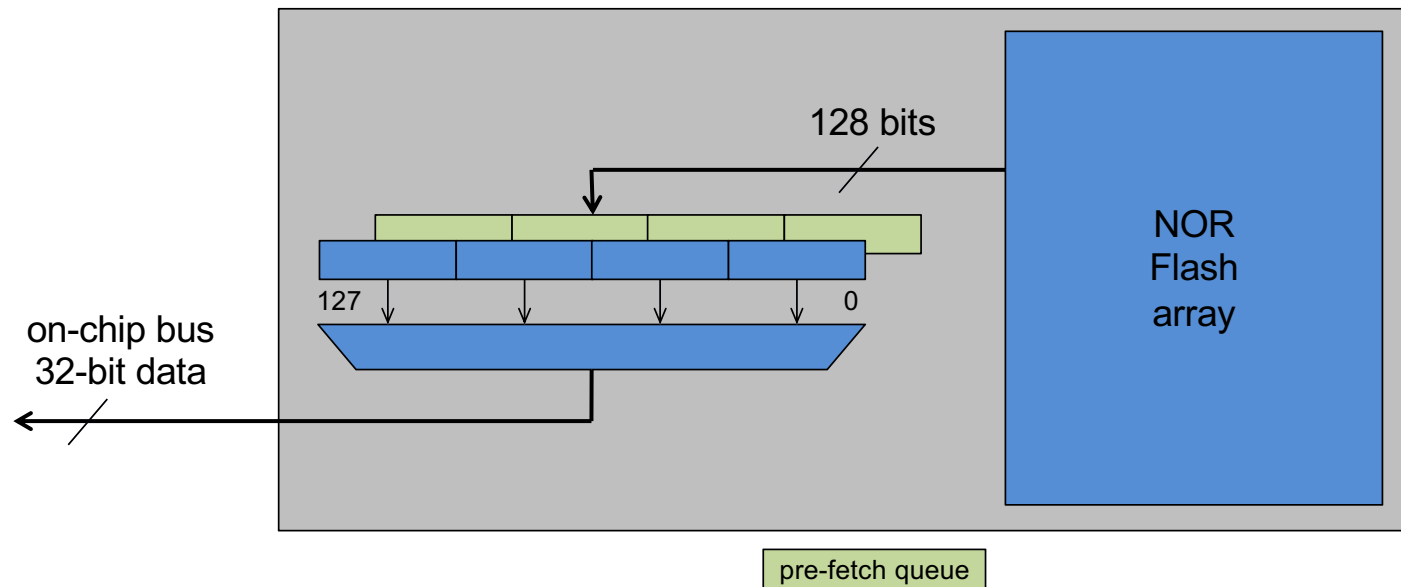- Read requires up to 8 Wait States¹⁾ on on-chip bus
- ST uses 128-bit buffer with pre-fetch queue
 - Reduces performance penalty when executing sequential instructions




Extending Our System

EXTERNAL MEMORY (OFF-CHIP)

■ Simplified Model STM32F429ZI

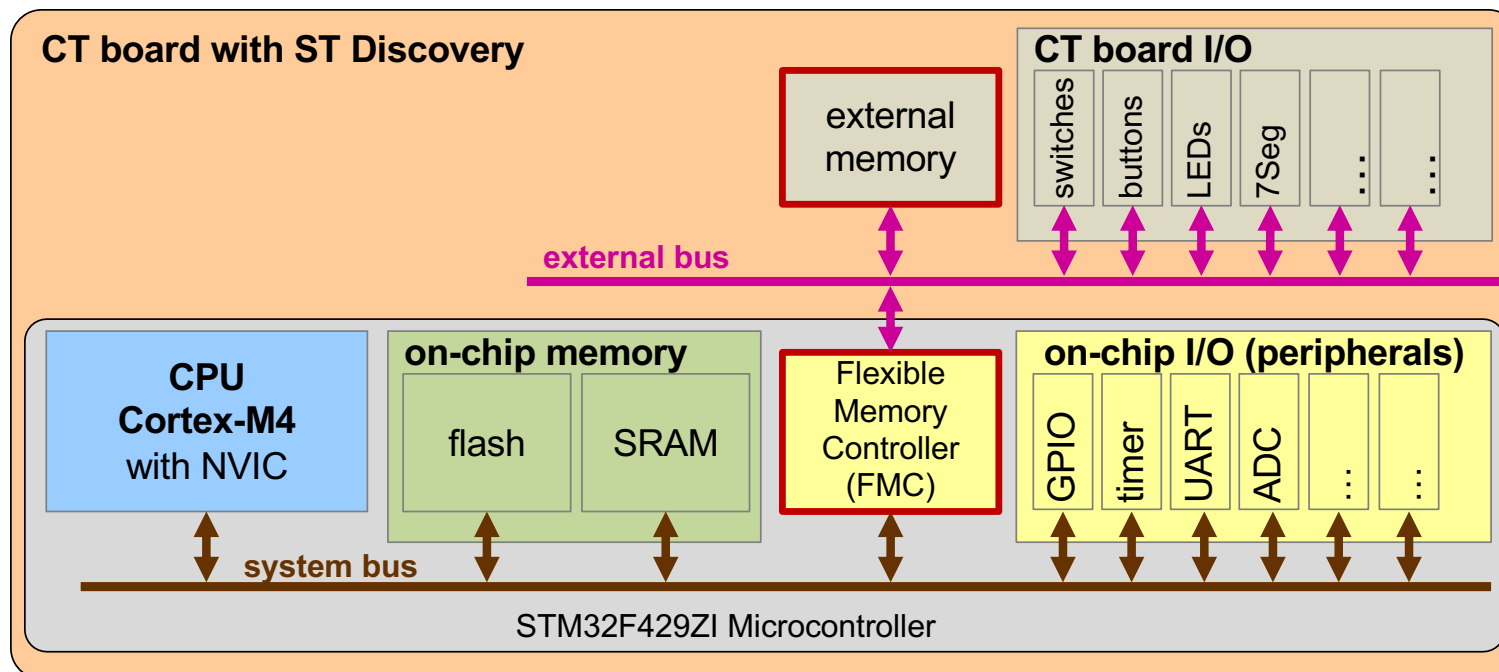
- On-chip system bus 32 data lines, 32 address lines and control signals
- External bus 16 data lines, 26 address lines and control signals



External Memory

■ Extend On-chip Memory

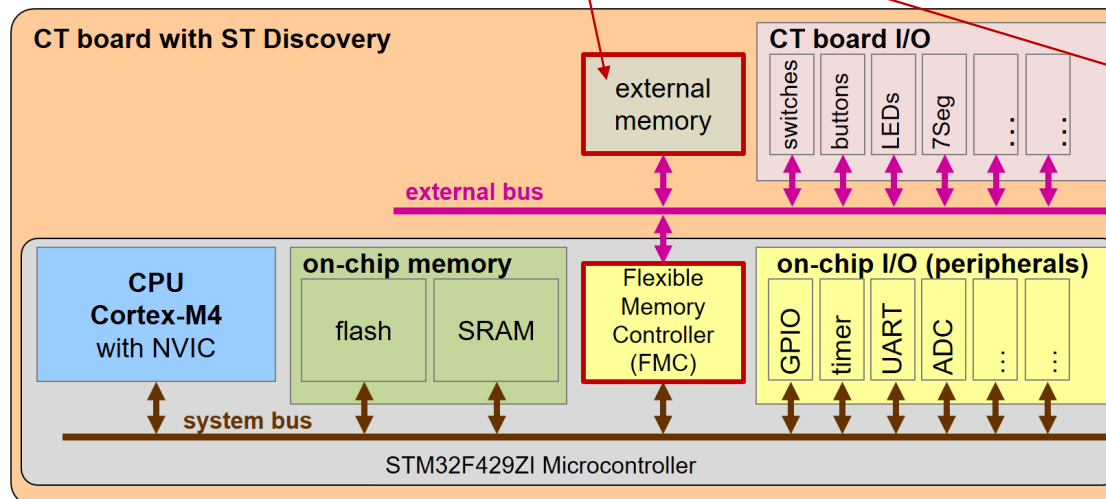- Flexible Memory Controller (FMC)
 - SRAM and NOR flash
 - Synchronous DRAM
 - NAND flash




0x0000'0000	system (boot)
0x1FFF'FFFF	
0x2000'0000	on-chip RAM
0x3FFF'FFFF	
0x4000'0000	ST peripherals
0x5FFF'FFFF	
0x6000'0000	CT board I/O
0x7FFF'FFFF	
0x8000'0000	
0x9FFF'FFFF	
0xA000'0000	external memory
0xBFFF'FFFF	
0xC000'0000	
0xDFFF'FFFF	
0xE000'0000	Cortex-M peripherals
0xFFFF'FFFF	

■ FMC – Configurable Bus Bridge

- Bridge between system bus and external bus
 - Slave on system bus
 - Master on external bus
- System bus accesses
 - In address range 0x6000'0000 to 0xDFFF'FFFF
 - Bridged to external bus
 - I.e. FMC initiates a bus cycle on external bus

 Number of data lines is a design decision and depends on the external memory device




■ Different Number of Data Lines Causes Bottleneck

- E.g. 32-bit (word) access to 8-bit external memory ¹⁾
 - Single access on system bus
 - Results in 4 accesses on external bus
→ increases access time by factor 4


■ Implementation FMC

 - CPU write to memory
 - Address and data stored in FMC FIFO buffer
 - Avoids wait for slow memory
 - Free system bus for other accesses
- CPU read from memory
 - System bus has to wait until external memory device provides data




■ Writing a 32-bit Word from System Bus (32 Data Lines)

 - to a 32-bit wide external memory (32 data lines)




- Word stored in FMC-FIFO
- System bus is released for other accesses
- FMC-FIFO content is transferred to external memory using 1 to 4 bus cycles

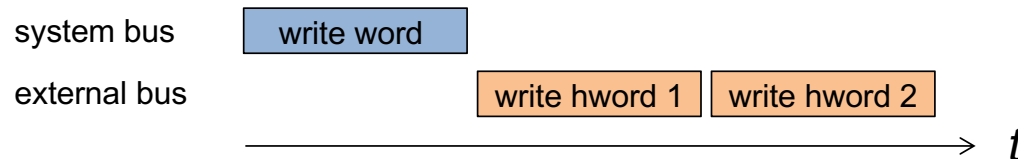- to a 16-bit wide external memory (16 data lines)




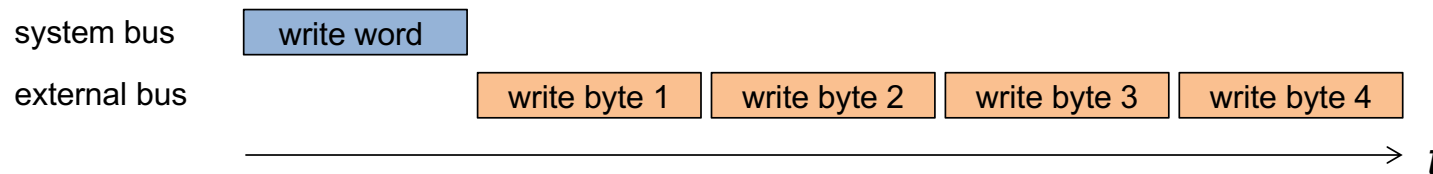- to an 8-bit wide external memory (8 data lines)




■ Reading a 32-bit Word from

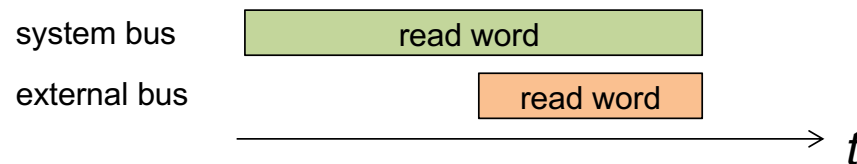
- a 32-bit wide external memory (32 data lines)



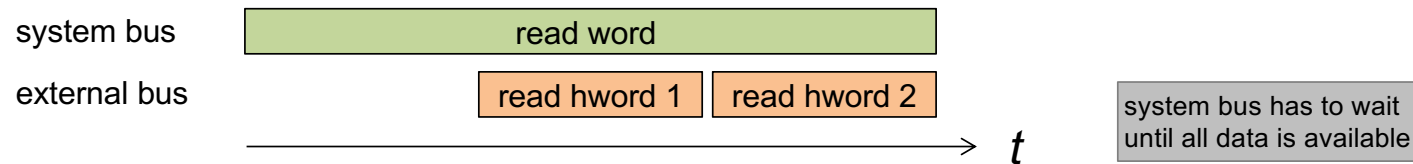- a 16-bit wide external memory (16 data lines)



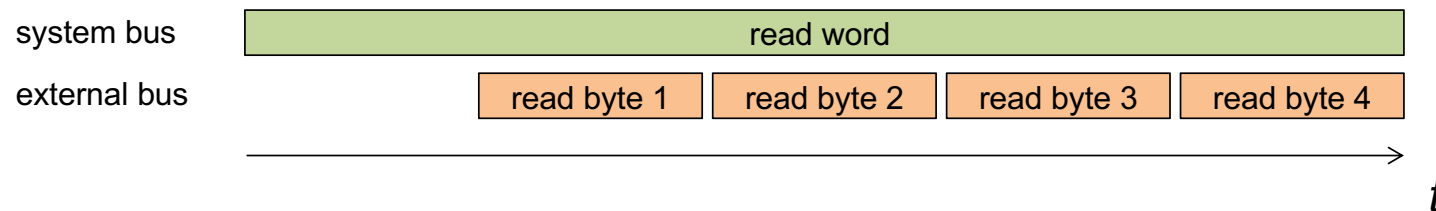- an 8-bit wide external memory (8 data lines)




■ FMC – Memory Banks¹⁾


- ST defined address ranges for each type of memory
- Organized in 6 banks
- Each bank allows connection of 4 devices
- Pins are multiplexed
 - Not possible to fully use all the banks simultaneously

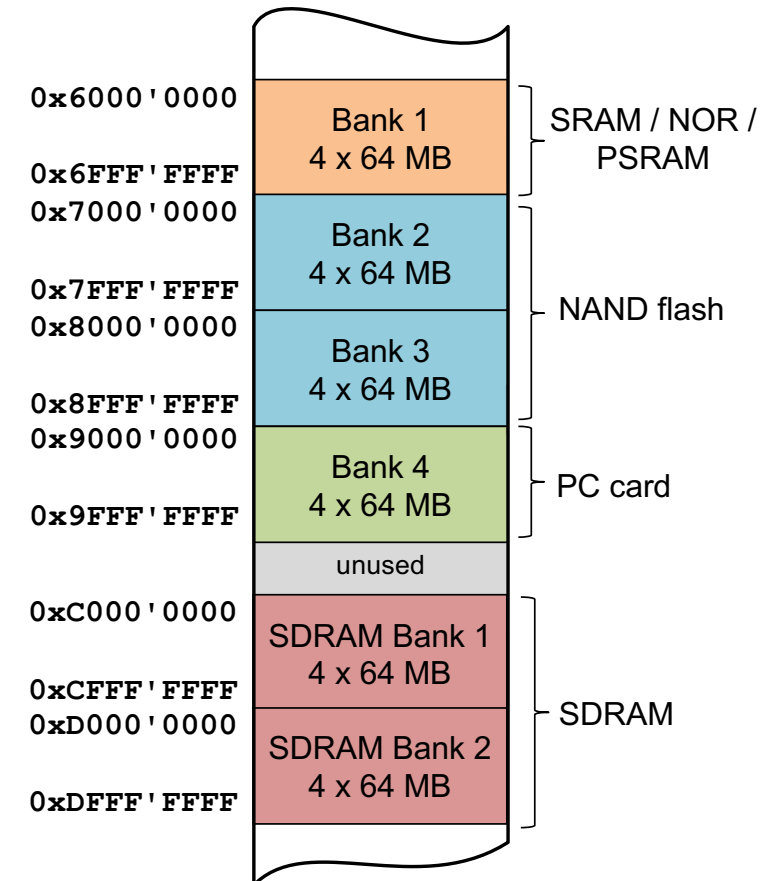1) An organizational unit of memory. Bank size is architecture dependent

Memory banks and their location in memory



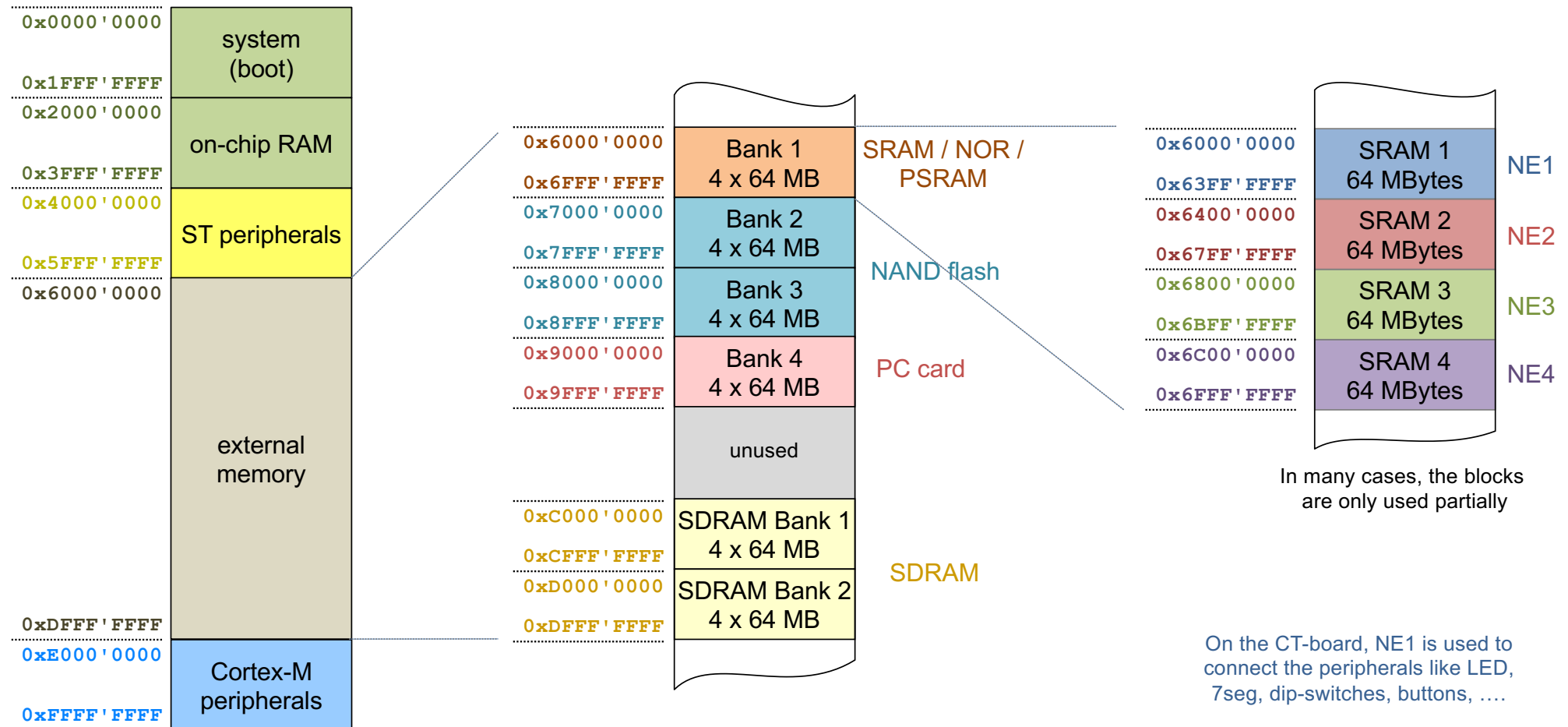Memory Banks and their Locations in Memory




Asynchronous SRAM

■ FMC – SRAM (Bank 1)

- Select one out of four SRAM devices
 - Address bits 27:26 → Encoded in signals NE[4:1]

A[27:26]	Enable	Memory Device
00	NE[1]	SRAM 1
01	NE[2]	SRAM 2
10	NE[3]	SRAM 3
11	NE[4]	SRAM 4

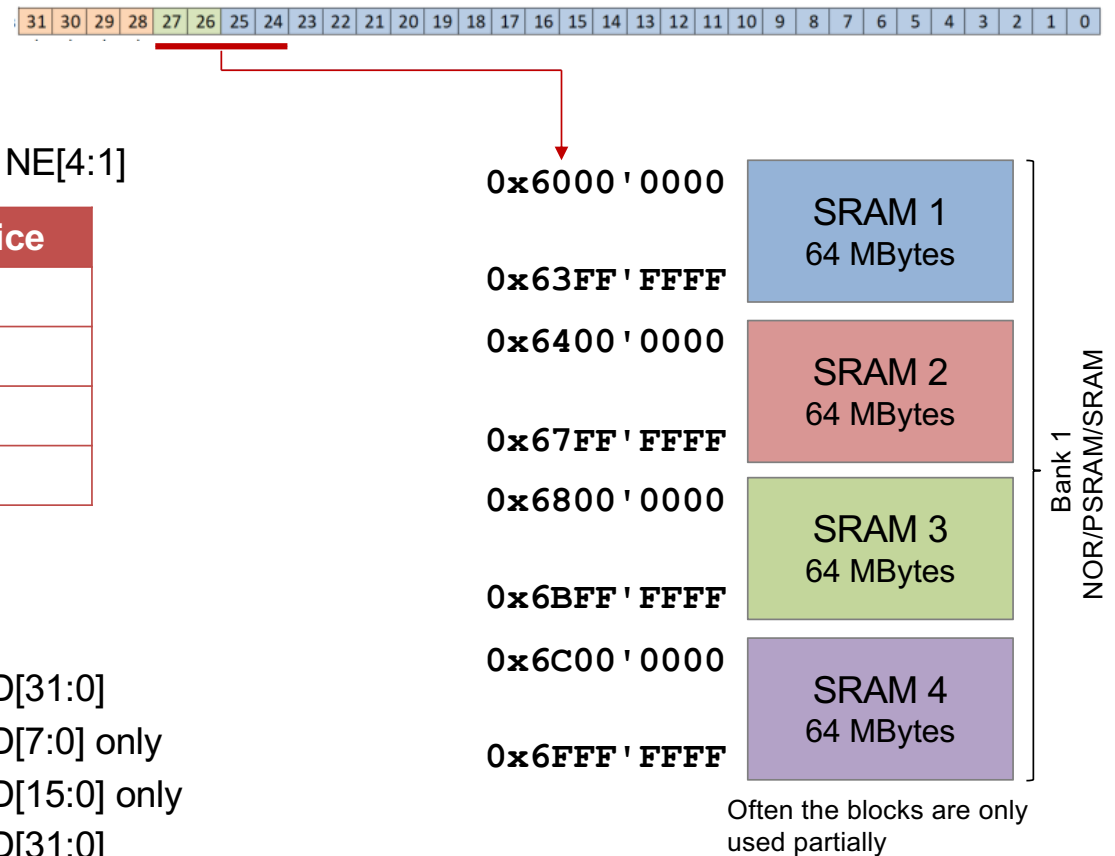- Data bus configured in control registers
 - Example
 - ▶ SRAM1 as 32-bit → D[31:0]
 - ▶ SRAM2 as 8-bit → D[7:0] only
 - ▶ SRAM3 as 16-bit → D[15:0] only
 - ▶ SRAM4 as 32-bit → D[31:0]



■ FMC Signals for SRAMs

- Prefix 'N' → active-low signal

FMC signal name	I/O	Function
A[25:0]	OUT	Address bus
D[31:0]	INOUT	Data bidirectional bus
NE[4:1]	OUT	Four enable lines ¹⁾
NOE	OUT	Output enable
NWE	OUT	Write enable
NBL[3:0]	OUT	Byte enable



see "Synchronous Bus" in slide set "Microcontroller Basics"

- Write accesses: NBL[3:0] indicate which bytes shall be updated (see lab)
 - Example 32-bit data bus D[31:0]
 - ▶ Word access → all four bytes NBL[3:0] = 0000b
 - ▶ Half-word access → two out of four bytes e.g. NBL[3:0] = 0011b
 - ▶ Byte access → one out of four bytes e.g. NBL[3:0] = 1011b

Asynchronous SRAM

■ Example 32K x 8-bit SRAM

 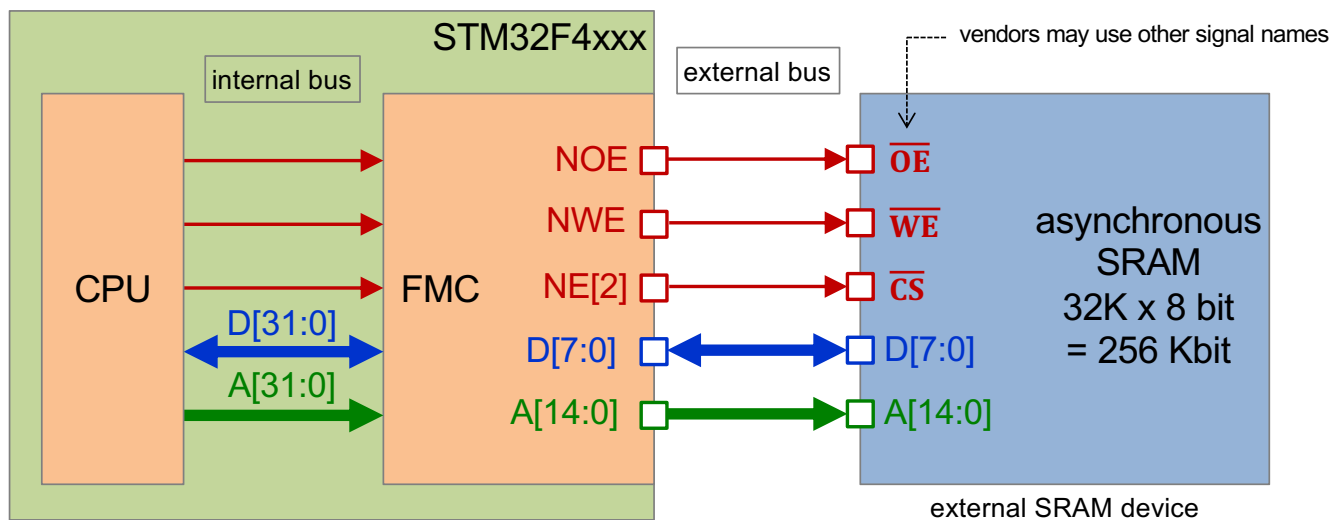
- Connecting an external 8-bit asynchronous SRAM device



Memory Banks and their Locations in Memory



■ An alternate view → use additional sheet

STM32F429 Flexible Memory Controller (FMC) Decoding

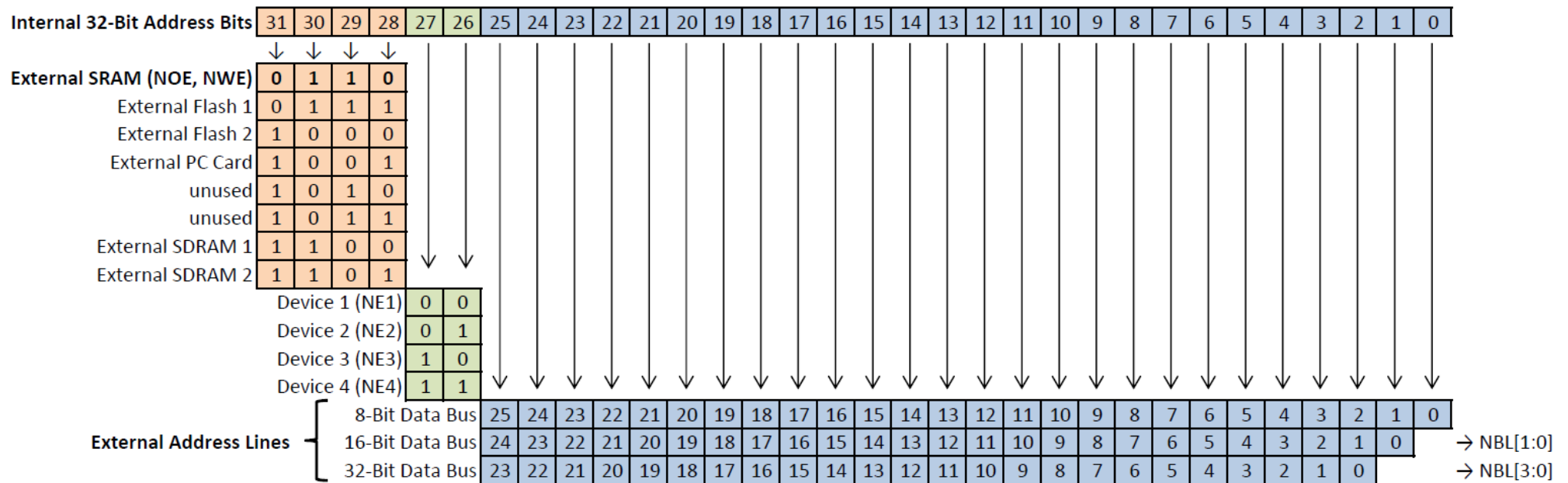


Connecting 8-16-32 Bit Memories to 32-bit Processors

8-bit wide memory

  

0x0 = b0000
0x1 = b0001
0x2 = b0010
0x3 = b0011
0x4 = b0100
0x5 = b0101
0x6 = b0110
0x7 = b0111
0x8 = b1000

32-bit wide memory

 

Connecting 8-16-32 Bit Memories to 32-bit Processors

8-bit wide memory

CPU Address	7	0
0x0	0x0	
0x1	0x1	
0x2	0x2	
0x3	0x3	
0x4	0x4	
0x5	0x5	
0x6	0x6	
0x7	0x7	
0x8	0x8	
0x9	0x9	
0xa	0xa	
0xb	0xb	

CPU Address	31	0
0x0		0x0
0x4		0x1
0x8		0x2


16-bit wide memory

CPU Address	15	0
0x0		0x0
0x2		0x1
0x4		0x2
0x6		0x3
0x8		0x4
0xa		0x5


Memory Address

Memory Address


Flexible Memory Controller

 

Flexible Memory Controller


 


Flexible Memory Controller

 


0x0 = b0000
0x1 = b0001
0x2 = b0010
0x3 = b0011
0x4 = b0100
0x5 = b0101
0x6 = b0110
0x7 = b0111
0x8 = b1000

 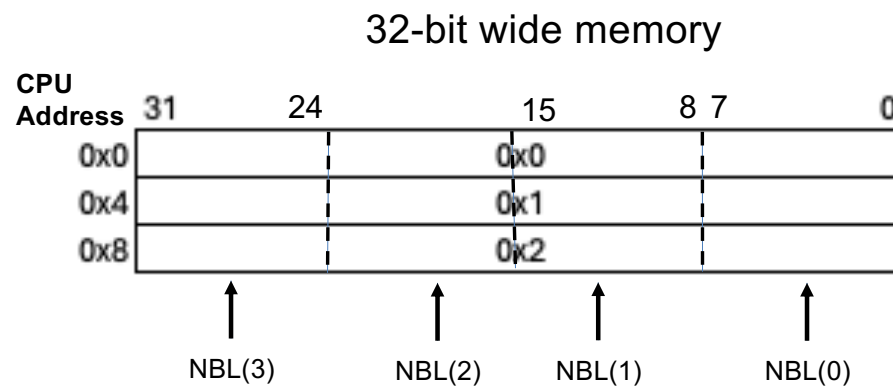Controlling Byte or Half Word Write Cycles





CT System Overview

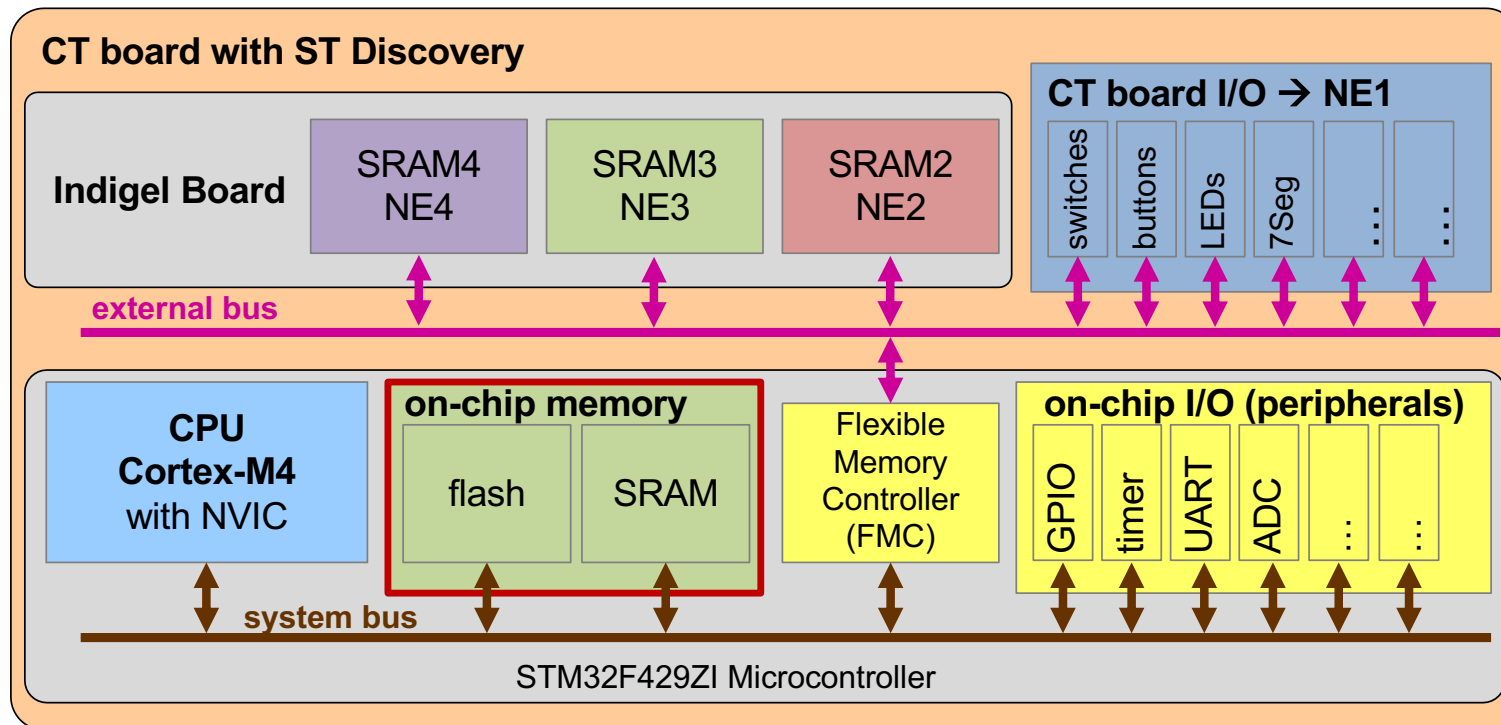

Asynchronous SRAM

■ Example (revisited)

 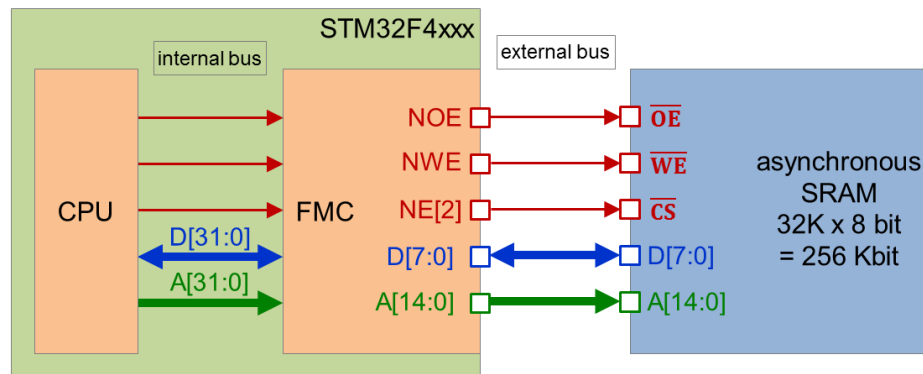
- Memory map of our previous 32K x 8 bit SRAM



Asynchrones SRAM


Read Access

Timing Waveform of Read Cycle No. 1⁽¹⁾

 

Write Access

 Timing Waveform of Write Cycle No. 1 (\overline{WE} Controlled Timing)^(1,2,4)




Asynchronous SRAM

■ Timing on External Bus


- As seen from the microcontroller

Figures from STM32F4xxx reference manual
p. 1591, chapter 37, Flexible Memory Controller

Read Access

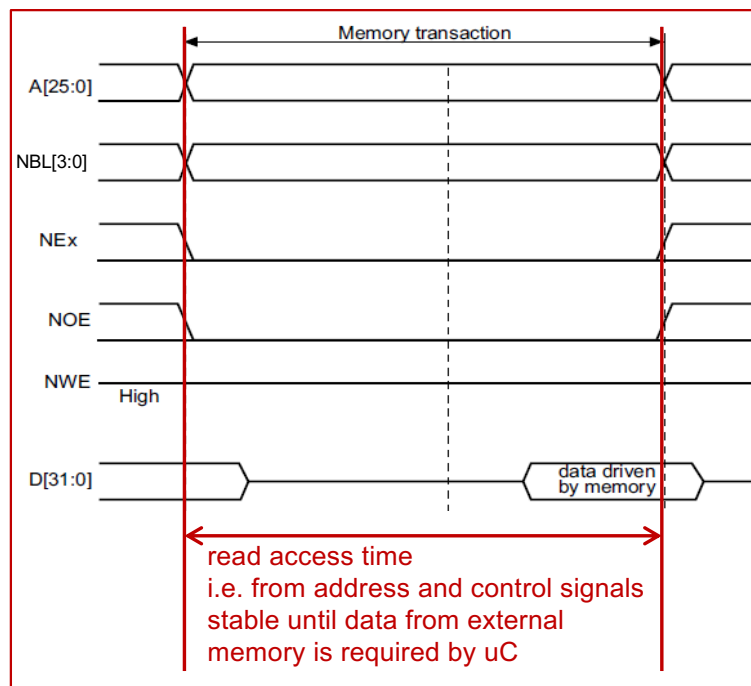


Write Access

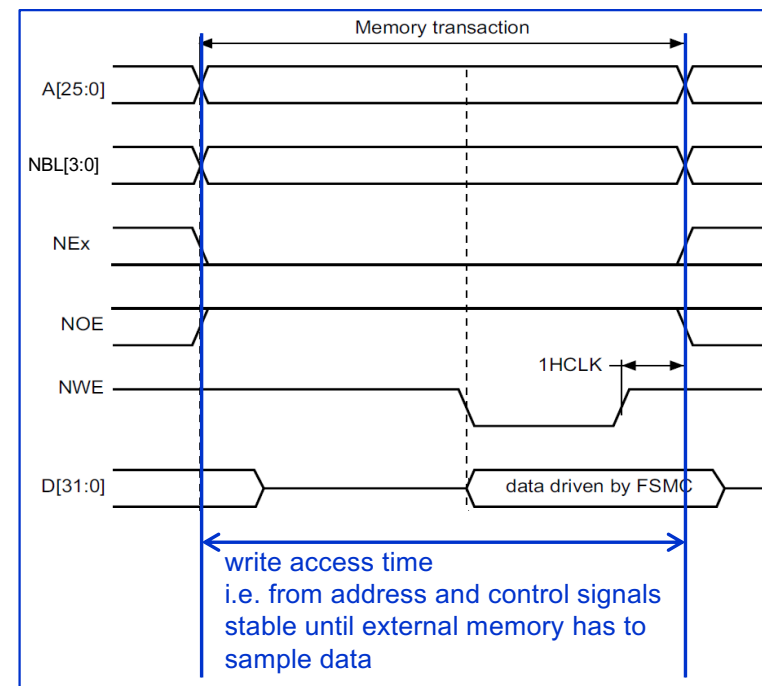

HCLK is the clock period of the CPU and the internal data bus

■ Configuration of FMC

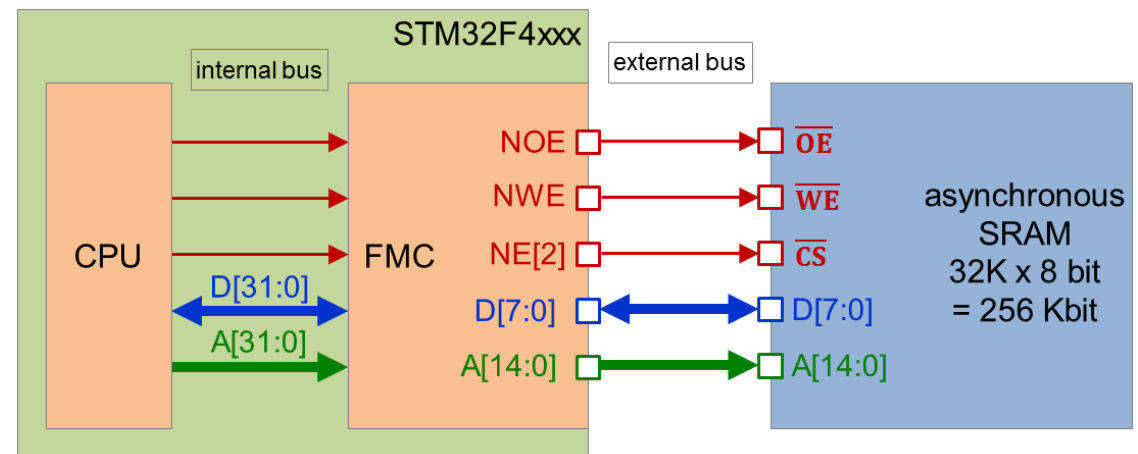- Location of FMC control registers
 - 0xA000'0000 – 0xA000'0FFF
- Configure FMC according to SRAM datasheet
 - Data bus size → 8-bit, 16-bit, 32-bit
 - Access times
 - and others



The FMC Registers allow configuration for many different memory types. However we only cover a few selected parameters for asynchronous SRAM.

Asynchronous SRAM

■ Configuring the FMC for SRAM

Table 291. FMC register map

Offset	Register	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0x00	FMC_BCR1	Reserved												CCLKEN	CBURSTRW	Reserved		ASYNCRWAIT	EXTMOD	WAITEN	WREN	WAITCFG	Reserved	WAITPOL	BURSTEN	Reserved	FACCEN	MWID	MTYP	MUXEN	MBKEN		
0x08	FMC_BCR2	Reserved												CBURSTRW	Reserved		ASYNCRWAIT	EXTMOD	WAITEN	WREN	WAITCFG	WRAPMOD	WAITPOL	BURSTEN	Reserved	FACCEN	MWID	MTYP	MUXEN	MBKEN			
0x10	FMC_BCR3	Reserved												CBURSTRW	Reserved		ASYNCRWAIT	EXTMOD	WAITEN	WREN	WAITCFG	WRAPMOD	WAITPOL	BURSTEN	Reserved	FACCEN	MWID	MTYP	MUXEN	MBKEN			
0x18	FMC_BCR4	Reserved												CBURSTRW	Reserved		ASYNCRWAIT	EXTMOD	WAITEN	WREN	WAITCFG	WRAPMOD	WAITPOL	BURSTEN	Reserved	FACCEN	MWID	MTYP	MUXEN	MBKEN			
0x04	FMC_BTR1	Res.	ACCMOD	DATLAT		CLKDIV		BUSTURN		DATAST					ADDHLD		ADDSET																
0x0C	FMC_BTR2	Res.	ACCMOD	DATLAT		CLKDIV		BUSTURN		DATAST					ADDHLD		ADDSET																
0x14	FMC_BTR3	Res.	ACCMOD	DATLAT		CLKDIV		BUSTURN		DATAST					ADDHLD		ADDSET																
0x1C	FMC_BTR4	Res.	ACCMOD	DATLAT		CLKDIV		BUSTURN		DATAST					ADDHLD		ADDSET																

00 8 bits
01 16 bits
10 32 bits
11 reserved

Use between 1 and 255 HCLK cycles during data phase.

Use between 1 and 15 HCLK cycles during address phase

Control register for SRAM1 → @ 0xA000'0000

Control register for SRAM2 → @ 0xA000'0008

Control register for SRAM3 → @ 0xA000'0010

Timing register for SRAM1 → @ 0xA000'0004

Control register for SRAM1 → @ 0xA000'0000

Control register for SRAM2 → @ 0xA000'0008

Control register for SRAM3 → @ 0xA000'0010

Timing register for SRAM1 → @ 0xA000'0004

00 8 bits
01 16 bits
10 32 bits
11 reserved

Use between 1 and 255 HCLK cycles during data phase.


Use between 1 and 15 HCLK cycles during address phase

■ ADDSET and DATAST


→ Adapt STM32F4 to the speed of the memory


- Configuring length of access cycles
- HCLK programmed to 84 MHz during start-up of CT-Board
 - HCLK = Frequency of CPU and internal bus

Read Access

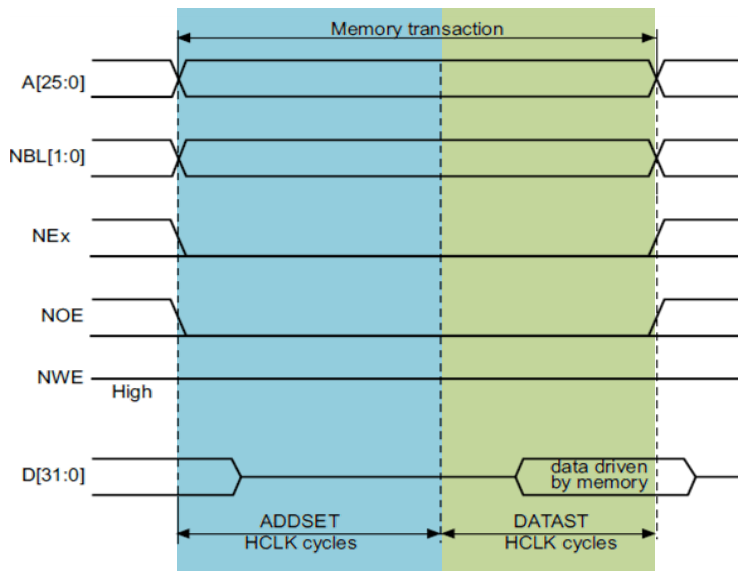

Write Access

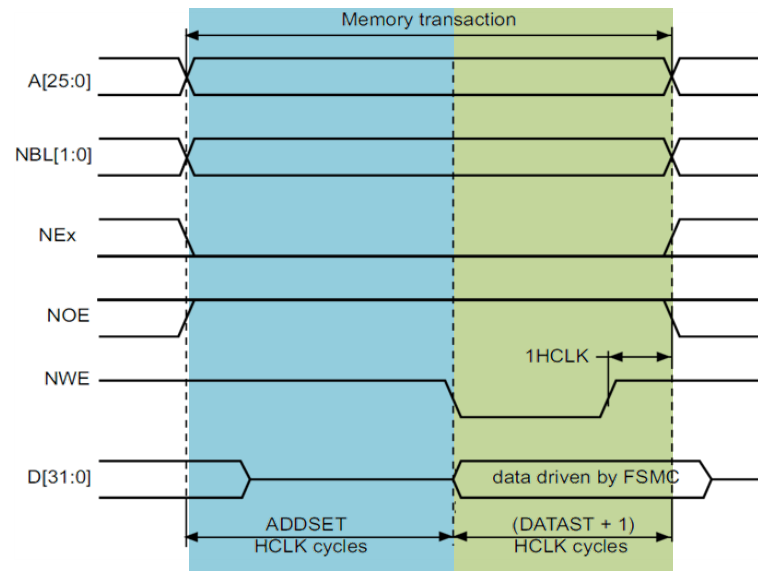

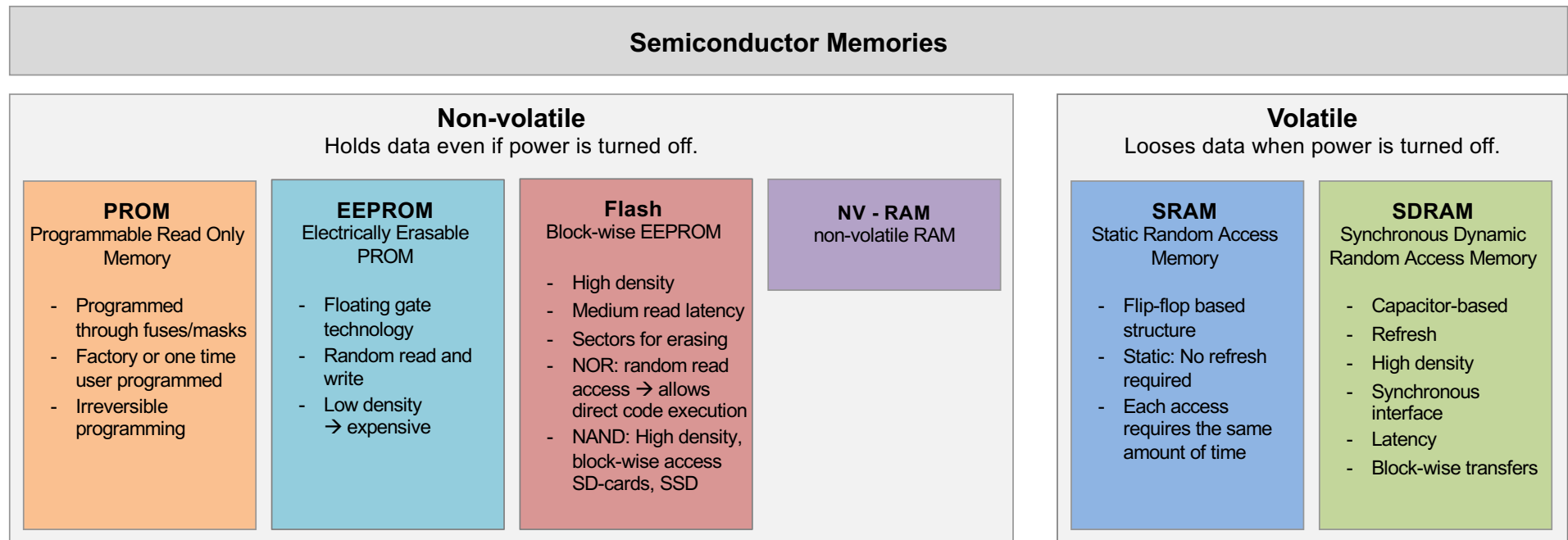


■ Flexible Memory Controller STM32

- Configurable bridge to connect external memories → e.g. asynchronous SRAM, NOR flashes, etc.


For Information Only

TRENDS AND FIGURES


SDRAM – Synchronous Dynamic RAM

 

SDR	Single Data Rate
DDR	Dual Data Rate uses rising and falling clock edge

 

Non-volatile Memory – Flash Densities

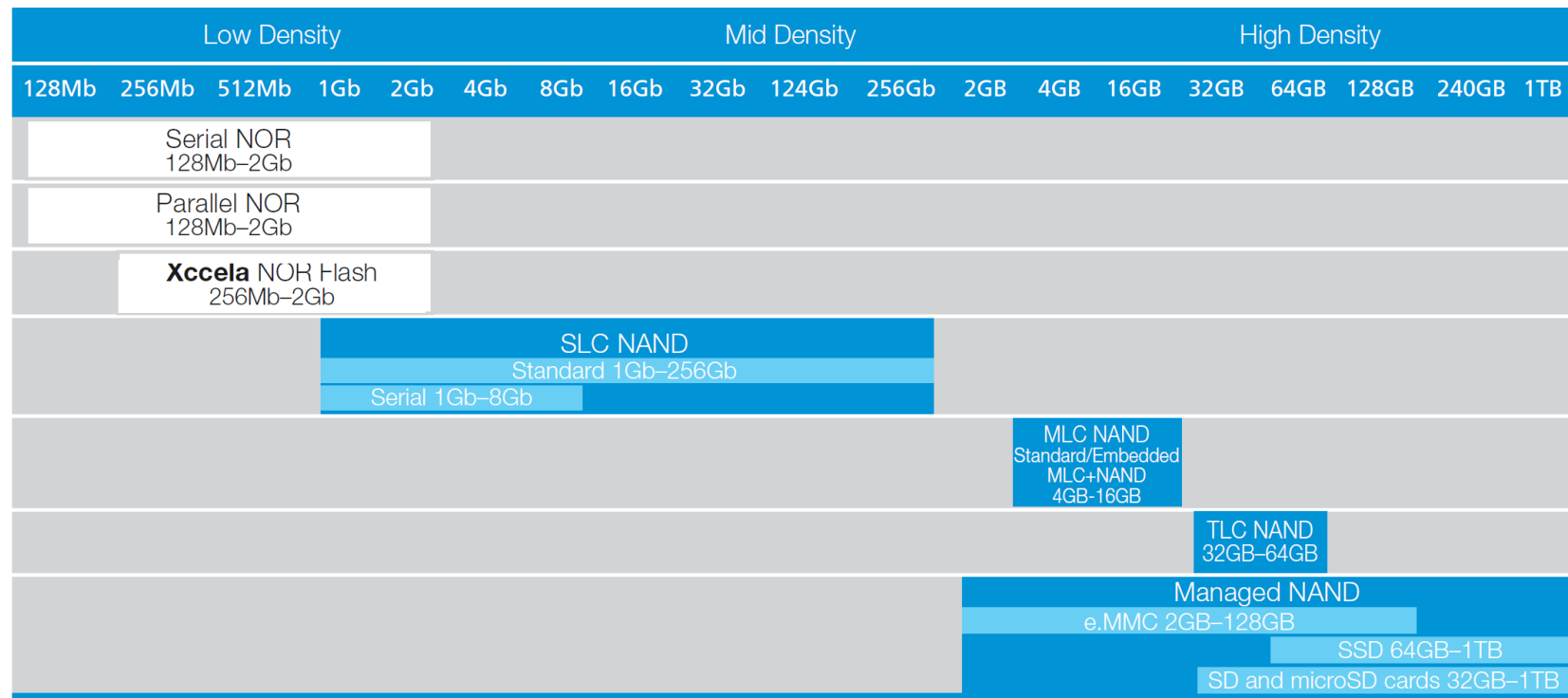

Managed NAND includes a controller for tasks like error correction.

SLC Single-Level Cell
MLC Multi-Level Cell
TLC Triple-Level Cell
MMC Multi-Media Card

Source: Micron NOR | NAND Flash Guide